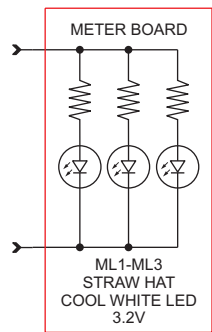



V_s = Voltage Source
 V_f = Forward Voltage
 I = current (0.02 amps)
 R_d = Dropping Resistance (ohms)
 Voltage Drop (V_d) = $V_s - V_f$
 Formula for resistance: $V_d/I=R_d$

PANEL METER PCB BOARDS



20 mA LED METER LIGHTS: PCB FV=3.2



Voltage Source V_s	Voltage Drop V_d	Dropping Resistor R_d	CLOSE
15	11.8	590	620
12	8.8	440	470
9	5.8	290	300
5	1.8	90	100
3	0	0	0

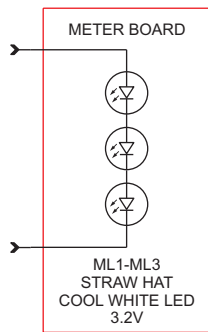



20 mA LED METER LIGHTS: PCB FV=9.6

Voltage Source V_s	Voltage Drop V_d	Dropping Resistor R_d	CLOSE
15	5.4	270	270
12	2.4	120	120
9	0	0	0

LEDS IN SERIES

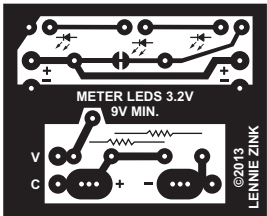
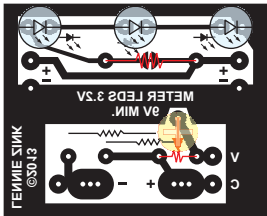



LEDS IN PARALLEL

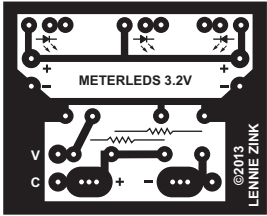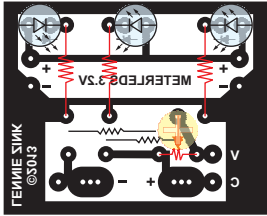


Mount trimmer on foil side of board for easy access.

LEDS IN SERIES

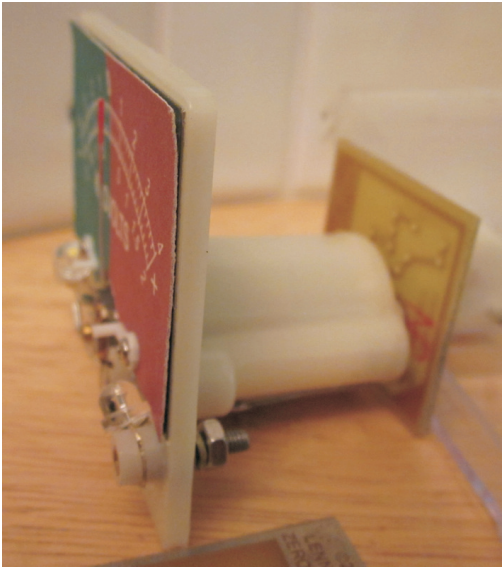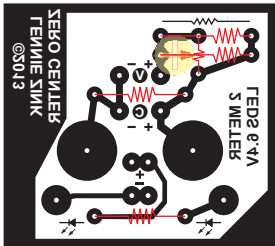

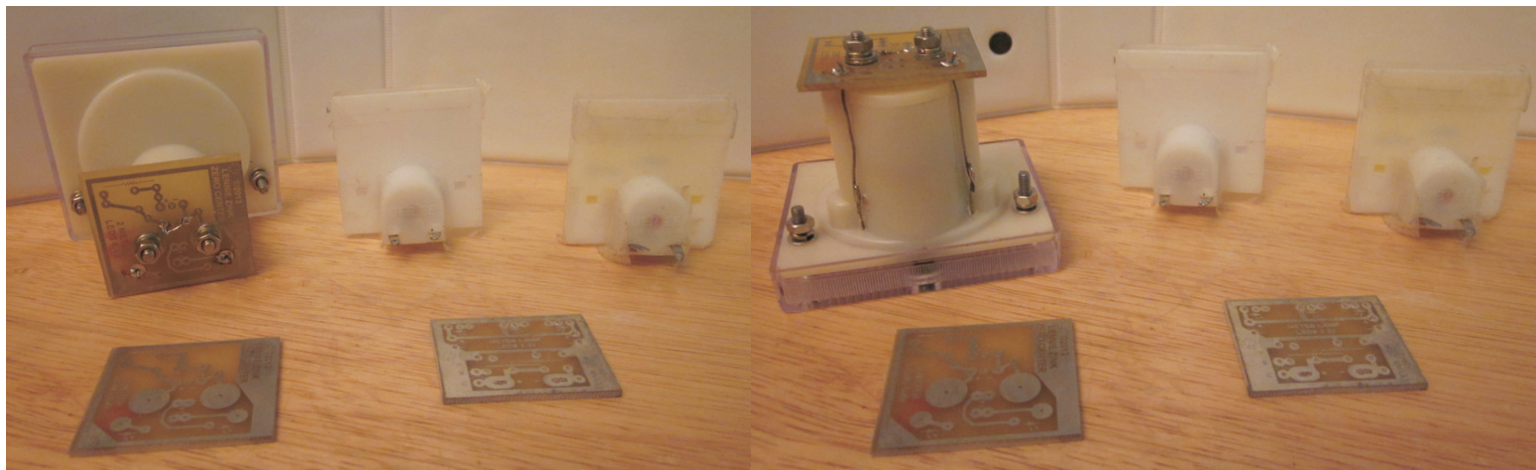

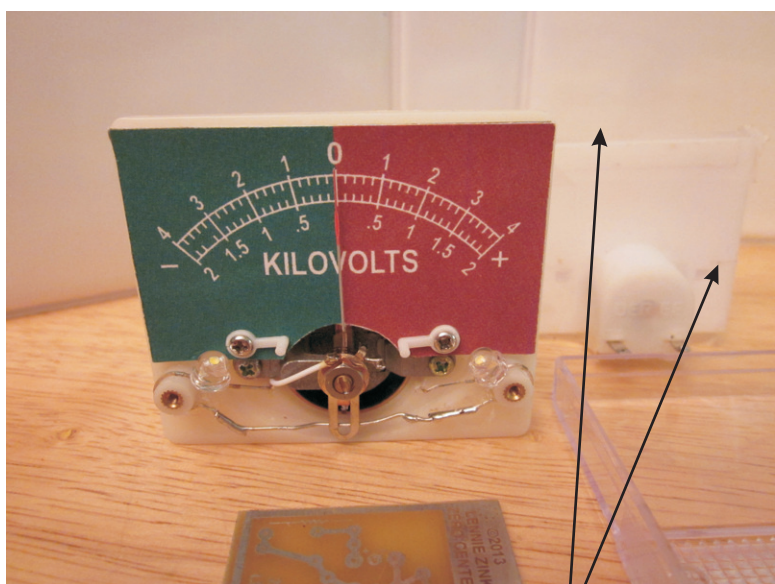See greater detail on meters my "Sferics Detector."



The cap on the tube of glue is a wire nut. I didn't notice that the cap was cracked when I bought it. Broke right through, it did!

This glue is remarkably removable. Peels off pretty well, but it attacks plastics.

Tape is used to protect the plastic.

