



The temperature sensor may be a different device if appropriate changes are made to the circuit. The first op-amp simply acts as a comparator which goes low when the temperature of the water pipe reaches a preset value. A feedback resistor gives the circuit a little hysteresis so that the water pipe must cool down a few degrees before the next shower is allowed. The amount of hysteresis determines how much time will elapse before the circuit resets. The 820k resistor sets the hysteresis. A lower value will increase the waiting time. The temperature set-point should be fairly high - near the maximum temperature - or else the reset time may be too long, even with low electrical hysteresis.

The 1N914 charges the capacitor quickly when the temperature drops back down below the reset temperature. This diode should be a low-leakage silicon diode.

The circuit is designed to operate a 24 VDC solenoid valve. The 1N4002 across the solenoid protects the power transistor from switching transients.

The power transformer may be wired to the light in the bathroom so that the solenoid is only activated when the light is on instead of continuously. This wiring will allow only cold showers when the lights are off, however!

A zener is shown connected between the power supply bridge and the three-terminal 15 volt regulator. The maximum rated voltage for most three-terminal regulators is 35 VDC but the rectified voltage from many smaller transformers may exceed this value when the loading is light. The zener may be selected to give about 25 volts at the regulator input. A 12 volt, 1 watt zener is a good first guess. Make sure that the input voltage does not drop below about 18 volts, however, or else the circuit will not operate properly. Reduce the zener voltage in this event.

Do not fail to connect the ground to the green wire. If you are not familiar with proper wiring practices then this device can be quite dangerous. Line voltages and water pipes make a deadly combination for the inexperienced. This device should be installed behind the wall with proper installation hardware. An electrician's approval is highly recommended. Do not attempt to build this device if you do not have the proper knowledge. Power the device from a circuit protected by a ground fault interrupter. Use a 24 VAC transformer designed for continuous household duty.

Oh, and do not use this device on any persons bigger than you!